

MODEL QUESTION PAPER

BSCO4/BSE4/BSET4

III Semester B.TECH Examination, August 2011 DIGITAL ELECTRONICS

Time: 3 Hours

Max. Marks: 75

GROUP A : Answer any three questions.

- Q.1 Draw and explain circuit diagram for BCD to 7 segment display decoder.
- Q.2 Draw and explain Edge Triggered S-R Flip Flop with their appropriate waveform.
- Q.3 Write down rules of Boolean algebra and prove Demorgan's theorems.
- Q.4 What is race ground condition? Explain how it is eliminated in master-slave JK Flip-Flop.
- Q.5 What do you mean by "counter"? Draw Binary Ripple Counter and explain basic principle with appropriate waveforms.

GROUP B : Answer any three questions.

- Q.6 Write a short note on Gray Code.
- Q.7 Subtract $(-64)_{10}$ from $(+32)_{10}$ using
 - (a) binary subtraction
 - (b) using its complement
 - (c) Two's complement.
- Q.8 What are basic differences between Boolean Algebra and Ordinary Algebra? Explain Boolean Expression.
- Q.9 Explain Nmos and Pmos logic families.
- Q.10 Draw and explain Combinational Logic Circuits. Give basic design steps to implement Combinational Logic Circuits.

GROUP C : All Questions are Compulsory.

Q.11 Fill in the blanks

- (i) The figure of merit of logic families is _____.
- (ii) $(111101100)_2 = (\text{_____})_8$.
- (iii) The purpose of clock input to flip flop is to _____.
- (iv) AND – OR – INVERT is provided with extra terminals to connect additional logic circuit called _____.
- (v) BCD code stands for _____.

Q.12 Multiple choice question

- (i) One of the following logic families is particularly suited for implementing LSI and VLSI functions.

- (a) PL (b) ECL
 (c) Scotty TTL (d) CMOS
- (ii) Following logic families does not use bipolar transistors _____.
 (a) COMS (b) DTC
 (c) RTL (d) TTL
- (iii) The excess-3 B CD code for $(1111)_2$ is _____.
 (a) 01001000 (b) $(10010)_2$
 (c) 00010101 (d) None of these
- (iv) The ring counter uses _____ flip flop for each stage in its sequence
 (a) One (b) Two
 (c) Three (d) None
- (v) $A + A' = ?$
 (a) 1 (b) 0
 (c) A (d) A'

Q.13 True or false

- (i) The n- channel MOS consists of lightly doped substrate of n – type silicon material.
- (ii) The heart of a DRAM is an array of single bit memory cells.
- (iii) A byte is equal to 8 bites.
- (iv) Flip-flops is stores 1 bit data.
- (v) A decade counter counts for ten days.
